

LøsningsforslagOppg. 1

$$a) \quad \underline{i_1} = \frac{V_1}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} = \frac{20}{20 + 10} \text{ A} = \frac{2}{3} \text{ A} = \underline{\underline{0.667 \text{ A}}}$$

$$\underline{v_2} = i_1 \cdot \frac{R_2 \cdot R_3}{R_2 + R_3} = \frac{2}{3} \cdot 10 \text{ V} = \frac{20}{3} \text{ V} = \underline{\underline{6.667 \text{ V}}}$$

$$b) \quad \begin{aligned} V_1 &= i_1 R_1 + i_2 R_2 \rightarrow 20 = i_1 \cdot 20 + i_2 \cdot 20 \\ I_1 &= -i_1 + i_2 \quad \quad \quad q = -i_1 + i_2 \end{aligned}$$


$$\left. \begin{aligned} 1 &= i_1 + i_2 \\ q &= -i_1 + i_2 \end{aligned} \right\} \quad \begin{aligned} 2i_1 &= 1 - q = -8 \Rightarrow \\ \underline{\underline{i_1}} &= \underline{\underline{-4.0 \text{ A}}} \end{aligned}$$

$$\underline{\underline{i_2}} = q + i_1 = 9 - 4 = \underline{\underline{5.0 \text{ A}}}$$

$$\underline{\underline{i_3}} = I_1 = \underline{\underline{9.0 \text{ A}}}$$

$$c) \quad C = \epsilon_0 \epsilon_r \frac{A}{t} = 8.854 \cdot 10^{-12} \cdot 3.8 \cdot \frac{1 \cdot 10^{-6}}{0.1 \cdot 10^{-6}} \text{ F}$$
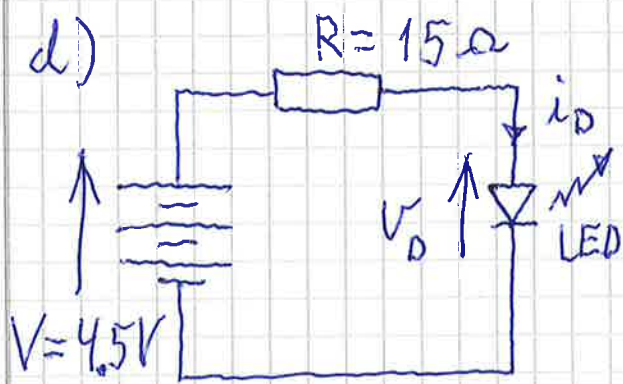
$$= 336 \cdot 10^{-12} \text{ F} = \underline{\underline{336 \mu\text{F}}}$$



$$V = R \cdot i_D + V_D$$

(2a)

Bråk arbetslinje

$$\underline{i_D = 0} : \underline{V_D = V = 4.5\text{V}}$$

$$\underline{V_D = 0} : \underline{i_D = \frac{V}{R} = \frac{4.5}{15}\text{A}}$$

$$= \underline{0.3\text{A}}$$

Fra figuren får vi: Se neste side

$$\underline{i_D \approx 0.10\text{A} = 100\text{mA}}$$

Se neste side →
erstatt

e) ~~$i_G = 0$~~ ~~$V_{GS} + i_D \cdot R_S = 15\text{V}$~~

~~$$V_{GS} = (15 - 3 \cdot 10^{-3} \cdot 3 \cdot 10^3)\text{V} = \underline{6.0\text{V}}$$~~

f) Ampers lov: $\oint \vec{H} \cdot d\vec{l} = \sum_{\text{alle } k} I_k$

Før toroiden, se figuren side 5 i formelsamlingen, velger vi en integrasjonsvei langs senterlinja (stiplet i figuren). \vec{H} og $d\vec{l}$ går i samme retning slik at (regner H konstant langs banen)

$$\oint \vec{H} \cdot d\vec{l} = \oint H dl = H \oint dl = N \cdot I$$

$$H \cdot 2\pi R = N \cdot I \Rightarrow \underline{\underline{H = \frac{N \cdot I}{2\pi R}}}$$

$$e) \quad V_m = 15 \text{ V}, T = 20 \text{ ms} \Rightarrow f = \frac{1}{T} = 50 \text{ Hz} \quad (26)$$

$$\theta = 360^\circ \cdot \frac{4}{20} = 72^\circ \quad \underline{\underline{v(t) = 15 \cdot \cos(2\pi 50t + 72^\circ)}}$$

$$\underline{\underline{V_{\text{eff}}}} = \frac{15}{\sqrt{2}} \text{ V} = \underline{\underline{10.61 \text{ V}}}$$

- g) (a) Asynkron (induksjon-) vekselstrømsmotor (3)
 (b) Synchron — " —
 (c) "Shunt"-koblet likestrømsmotor
 (d) Serie-koblet — " —


h) Se læreboka / forelesningspresentasjon

$$i) \omega_m = n_m \frac{2\pi}{60} = 1450 \cdot \frac{2\pi}{60} \text{ rad/s} = \underline{\underline{151.84 \text{ rad/s}}}$$

$$T_{\text{tot}} = \frac{P_{\text{ut}}}{\omega_m} = \frac{100 \cdot 745.7}{151.84} \text{ Nm} = \underline{\underline{491.1 \text{ Nm}}}$$


j) · See læreboka

Til d)

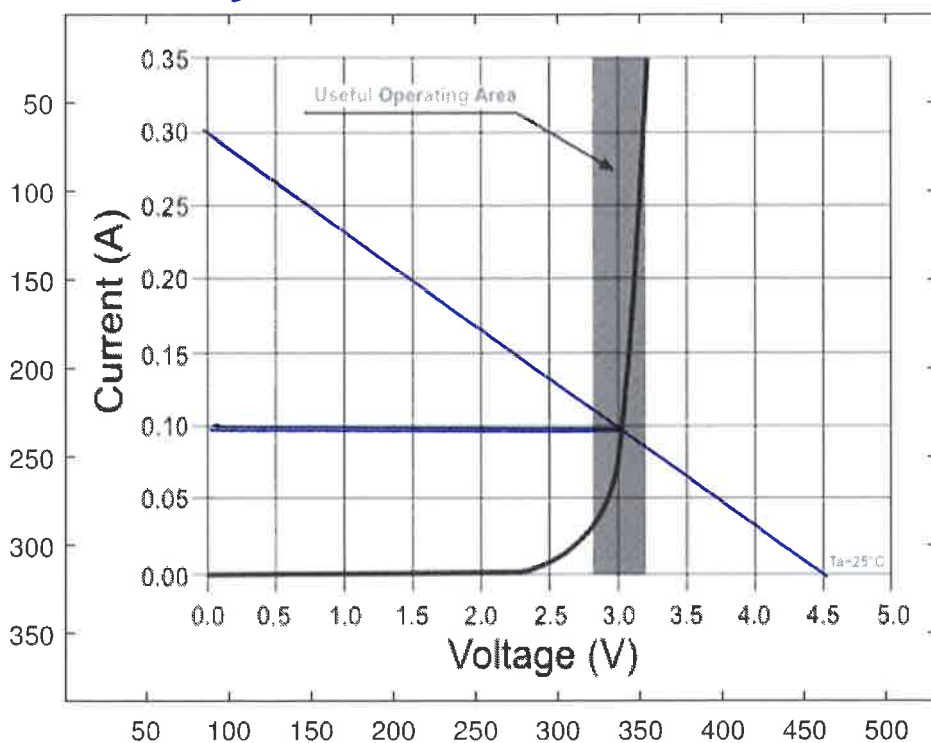

Oppg. 2 a)

(4)

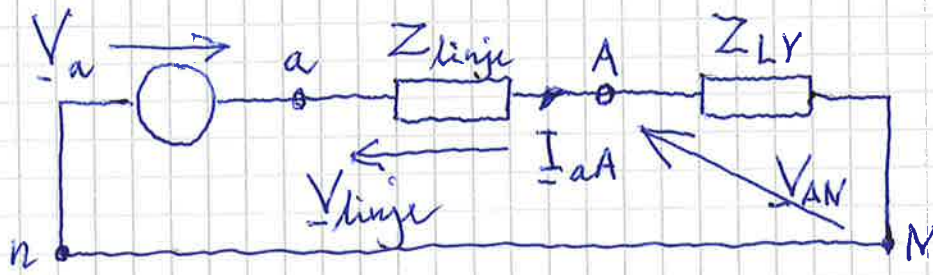

$$Z_{LY} = \frac{Z_A}{3} = \frac{Z_L}{3} = \frac{4.5 + j1.8}{3} = (1.5 + j0.6) \Omega$$

Fasespenninger: $|V_{AN}| = \frac{1}{\sqrt{3}} \cdot |V_{AB}| = \frac{762.1}{\sqrt{3}} V$
 $= 440 V$

For et symmetrisk trefasesystem har vi da

$$\underline{V_{AN}} = 440V \angle 0^\circ$$

b)

$$\underline{I_{aA}} = \frac{\underline{V_{AN}}}{Z_{LY}} = \frac{440}{1.5 + j0.6} A = (253 - j101) A$$

$$= \underline{272 A \angle -22^\circ}$$

c) $\underline{V_{line}} = \underline{I_{aA}} Z_{line} = 272 A \angle -22^\circ \cdot \underbrace{(0.03 + j0.04)}_{0.05 \Omega \angle 53^\circ}$
 $= (11.6 + j7.08) V$
 $= \underline{13.6 V \angle 31^\circ}$

$$\underline{V_a} = \underline{V_{line}} + \underline{V_{AN}} = 11.6 + j7.08 + 440$$

$$= (452 + j7.1) V = \underline{452 V \angle 0.9^\circ}$$


$$d) \quad \underline{I}_{ZL} = \frac{\underline{V}_{AB}}{Z_L} = \frac{762.1 \angle 30^\circ}{4.5 + j1.8} = (156 + j22.4) \text{ A} \\ = \underline{157 \text{ A} \angle 8^\circ} \quad (5)$$

$$\underline{|\underline{I}_{ZL}| \cdot \sqrt{3}} = 157 \cdot \sqrt{3} \text{ A} = 272 \text{ A} = \underline{|\underline{I}_{aA}|}$$




Tallverdien til linjestrømmen er $\sqrt{3}$ tallverdien til fasestrømmen for en Δ -kobling!

Vinkelen mellom dem er $\underline{30^\circ = 22^\circ + 8^\circ!}$

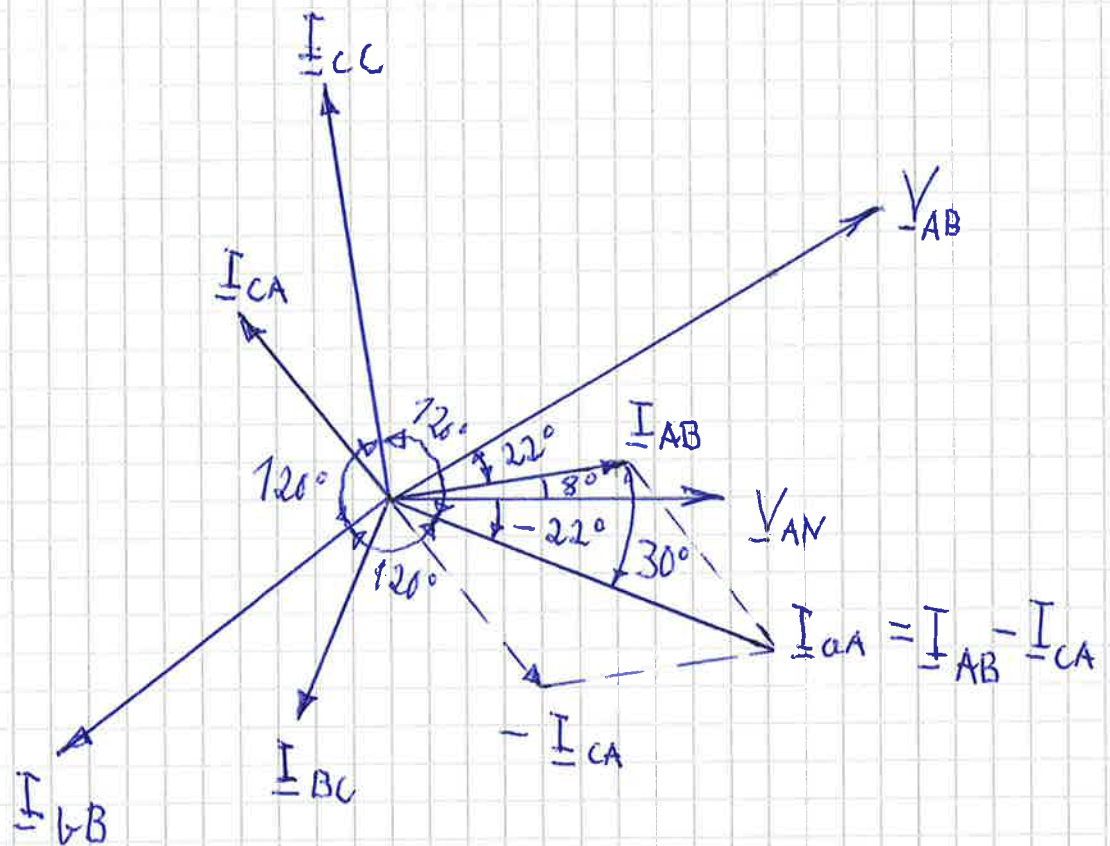Dette gjelder for et symmetrisk trefase-system.



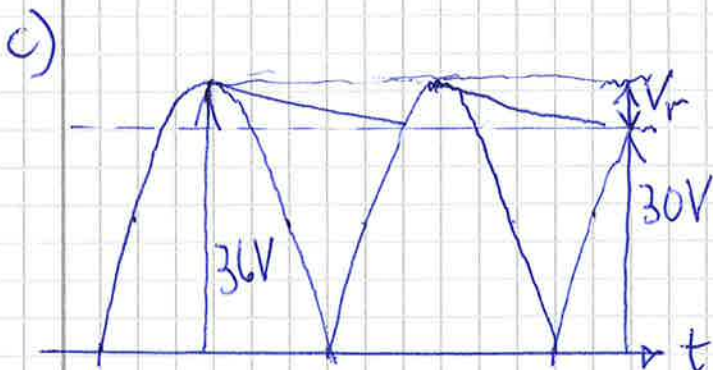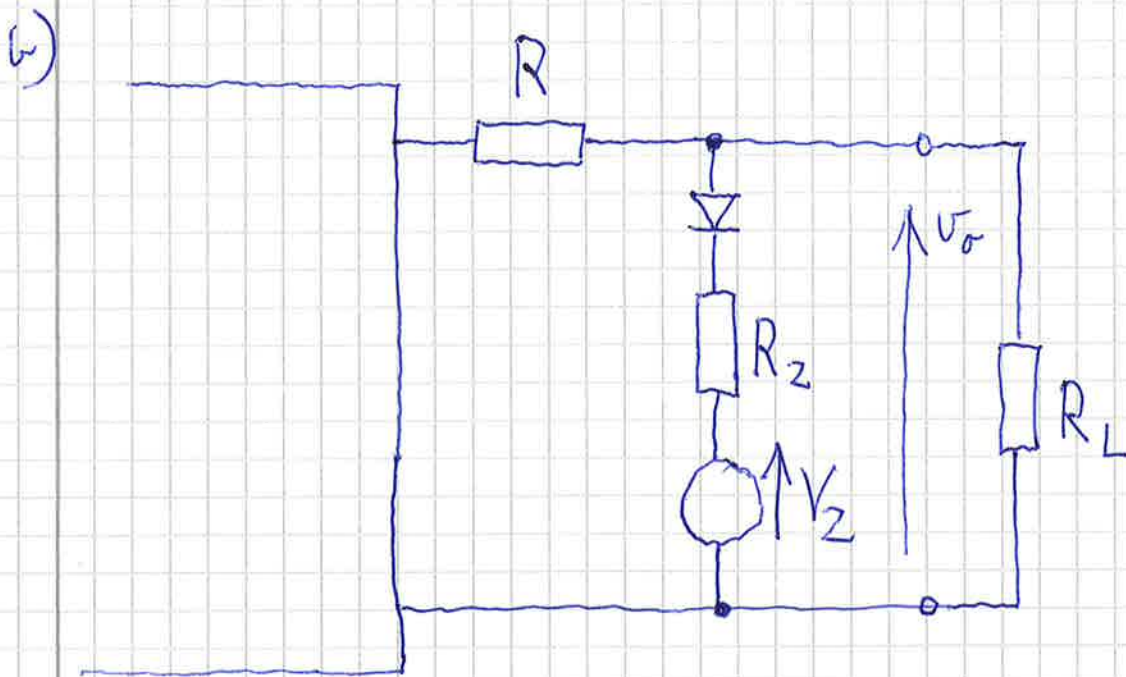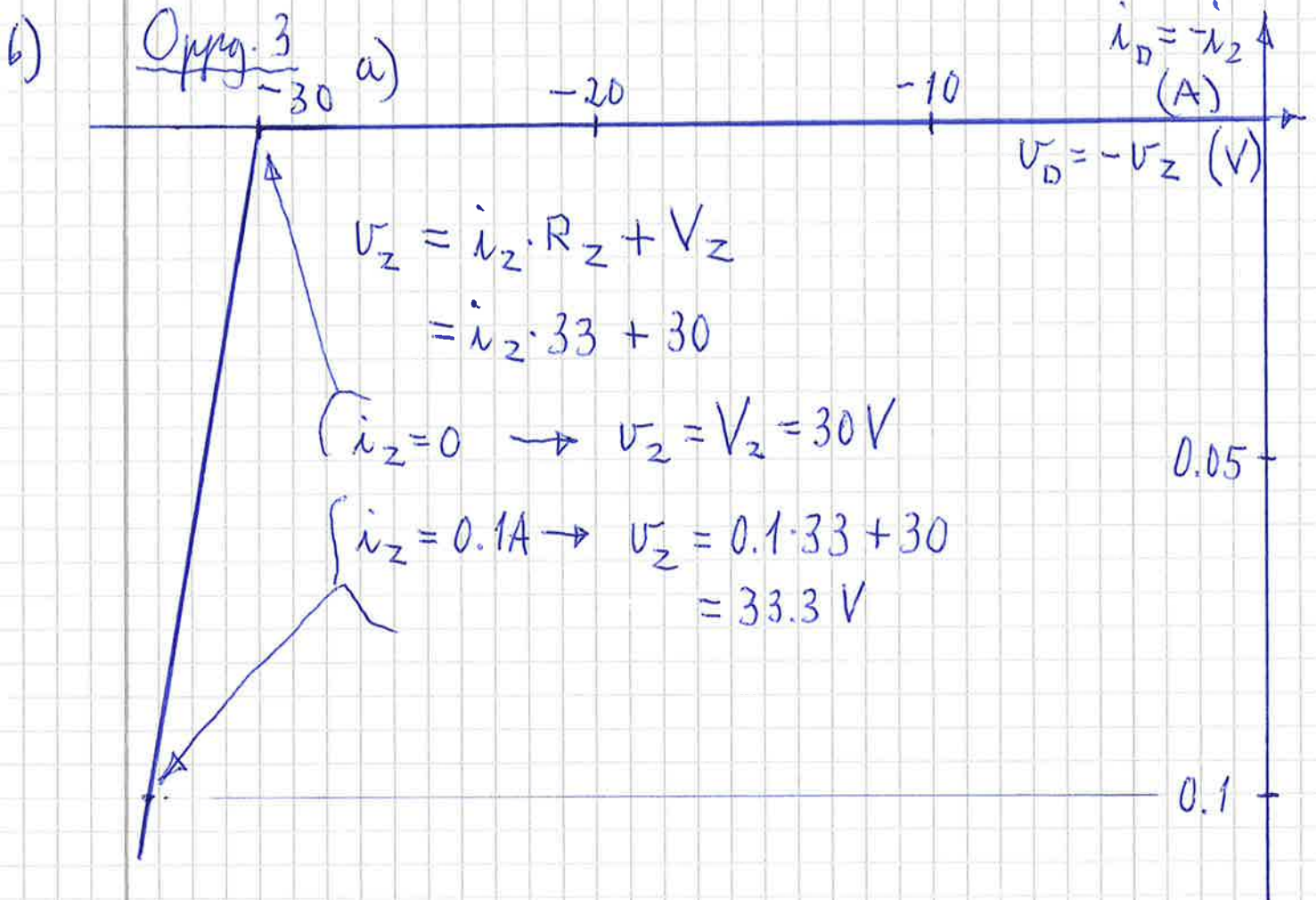Viserdiagram for strømmene. Spenningen for fase A er også med som referanse.



For at zenerdioden skal lede i bakoverretning må

$$\underline{V_r < 36 - 30 = 6 \text{ V}}$$

7) Oppg. 4 a) $n_s = \frac{120f}{p} = \frac{120 \cdot 50}{6} \text{ } \circ/\text{min} = \underline{\underline{1000 \text{ } \circ/\text{min}}}$ (7)

b) $n_m = 995 \text{ } \circ/\text{min}$ for $T_{\text{ut}} \approx 500 \text{ Nm}$

$$s = \frac{n_s - n_m}{n_s} = \frac{1000 - 995}{1000} = \underline{\underline{0.005}}$$

c) "Pull-out" momentet er maksimum moment avlest fra kurven:

$T_{\text{pullout}} \approx 2200 \text{ Nm}$ ved ca. $940 \text{ } \circ/\text{min}$.

d) Fasesstrømmen ved start.

Ved start er $n_m = 0$, $s = 1$

Regner først ut impedansen når $s = 1$.

$$Z_r' = R_r' + jX_r' = (0.04 + j0.2) \Omega$$

$$Z_{eq} = \frac{Z_m \cdot Z_r}{Z_m + Z_r} = \frac{j8 \cdot (0.04 + j0.2)}{j8 + 0.04 + j0.2} = 0.0381 + j0.1953$$

$$Z_{\text{tot}} = Z_s + Z_{eq} = R_s + jX_s + Z_{eq} = 0.48 + j0.3 + 0.0381 + j0.1953$$

$$= 0.518 + j0.495$$

$$I_{s, \text{start}} = \frac{V_s}{Z_{\text{tot}}} = \frac{440}{0.518 + j0.495} \text{ A} = (443.7 - j424.2) \text{ A}$$

$$= \underline{\underline{614 \text{ A} \angle -43.7^\circ}}$$

8)

$$e) P_{cu} = P_{cus} + P_{cur} = 3 \cdot [R_s \cdot |I_s|^2 + R_r' \cdot |I_r'|^2] \quad (8)$$

$$= 3 \cdot [0.48 \cdot 71.665^2 + 0.04 \cdot 50.045^2] \text{ W}$$

$$= \underline{\underline{7696 \text{ W}}}$$

f) For å finne virkningsgraden trenger vi inn- og utgangseffekt.

$$P_{inn} = \text{real} \{ 3 \cdot \underline{V}_s \cdot \underline{I}_s^* \}$$

$$= \text{real} \{ 3 \cdot 440 \cdot 71.665 (\cos(44.47^\circ) - j \sin(-44.47^\circ)) \}$$

$$= 3 \cdot 440 \cdot 71.665 \cdot \cos(44.47^\circ) \text{ W}$$

$$= \underline{\underline{67507 \text{ W}}}$$

$$R_{ut} = \frac{1-s}{s} \cdot R_r' = \frac{1-0.005}{0.005} \cdot 0.04 \Omega = 7.96 \Omega$$

$$P_{utr.} = 3 \cdot R_{ut} \cdot |I_r'|^2$$

$$= 3 \cdot 7.96 \cdot 50.045^2 \text{ W} = 59808 \text{ W}$$

$$P_{ut} = P_{utr.} - P_{rst} = (59808 - 6000) \text{ W} = \underline{\underline{53808 \text{ W}}}$$

$$\eta = 100\% \cdot \frac{P_{ut}}{P_{inn}} = 100\% \cdot \frac{53808}{67507} = \underline{\underline{79.7\%}}$$

(Effekt)faktor:

$$\text{pf} = \cos(-44.47^\circ) = \underline{\underline{0.714}}$$

$$\underline{I}_s = 71.665 \text{ A} \angle -44.47^\circ, \underline{V}_s = 440 \text{ V} \angle 0^\circ$$

Oppg. 5 a) $n_m = n_s = \frac{120 \cdot f}{p} = \frac{120 \cdot 50}{8} = \underline{\underline{750 \text{ /min}}}$ (4)

b) $|I_a| = \frac{P_{\text{inn}}}{3 \cdot V_a \cdot \cos(\theta)}$ Utten tap er
 $P_{\text{inn}} = P_{\text{ut}} = 500 \cdot 745.7 \text{ W}$
 $= \frac{500 \cdot 745.7}{3 \cdot 480 \cdot 0.9} \text{ A} = 287.7 \text{ A}$

$\theta = \text{Arccos}(0.9) = 25.84^\circ$ Induktiv \Rightarrow

$\underline{\underline{I_a = 287.7 \text{ A} \angle -25.84^\circ}}$

c) $Z_s = jX_s = j0.5$


$\underline{\underline{E_r = V_a - I_a \cdot Z_s = 480 - 287.7 \angle -25.84^\circ \cdot 0.5 \angle 90^\circ}}$
 $= (417.3 - j129.5) \text{ V} = \underline{\underline{437 \text{ V} \angle -17.2^\circ}}$

$\delta = 17.2^\circ$ Momentvinkelen

Se vektor diagram på neste side.

d) Når effekten er konstant flytter den induerte spenningen seg langs en horisontal linje, se vektor diagrammet. Den nye momentvinkelen blir da

$\underline{\underline{\delta_2 = \text{Arcsin}\left(\frac{V_v}{|E_{r2}|}\right)}}$ $V_v = |E_{r1}| \cdot \sin(\delta_1)$
 $= \text{Arcsin}\left(\frac{129.5}{570}\right) = 437 \cdot \sin(17.2^\circ)$
 $= \underline{\underline{13.1^\circ}} = 129.5 \text{ V}$

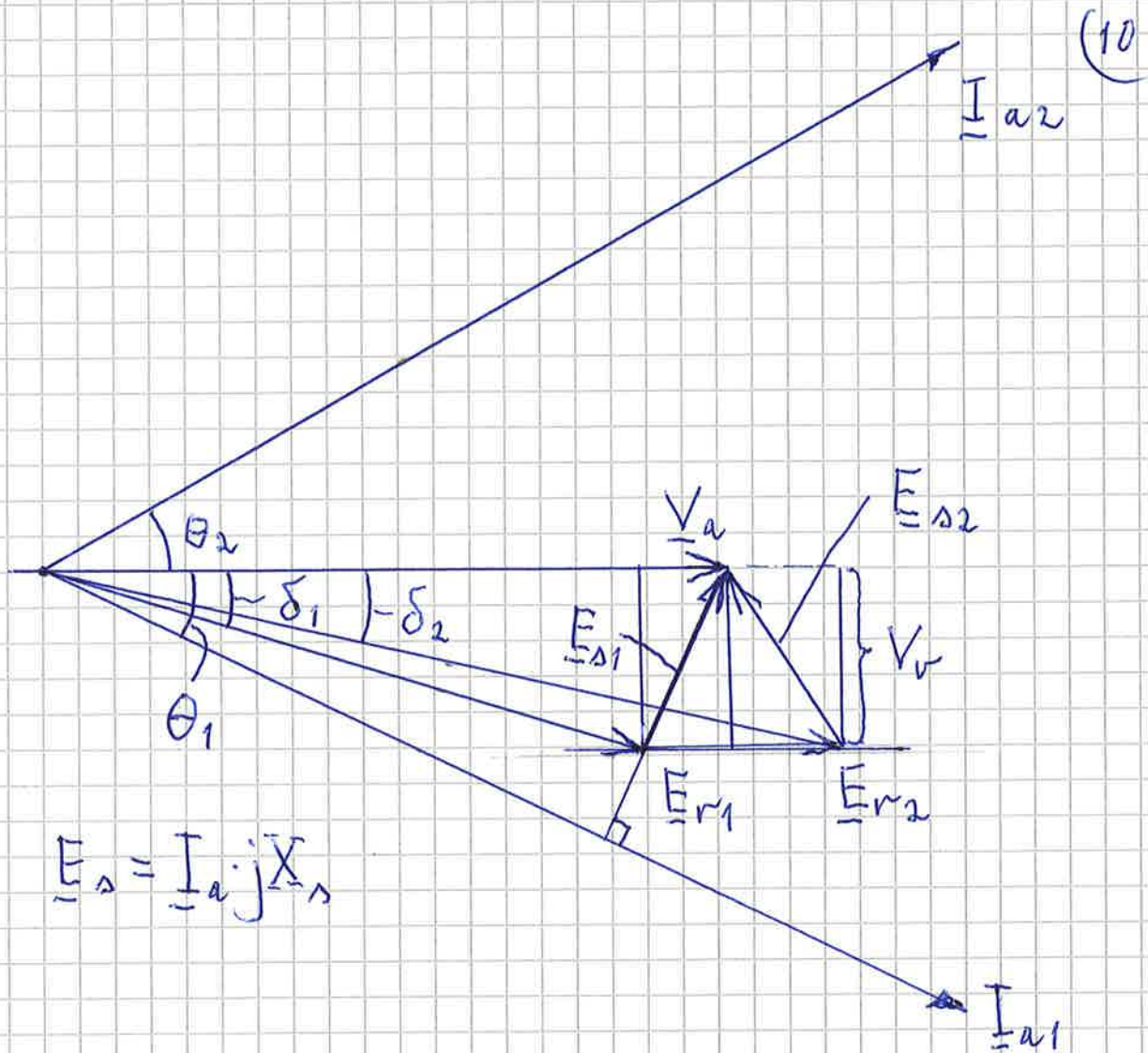

$$\underline{E}_s = \underline{I}_a \cdot jX_s$$

e) $V_v = E_{r2} \cdot \cos \delta_2 = 555.1 \text{ V}$

$$\underline{E}_{s2} = -(V_v - V_a) + jV_v = -(555.1 - 480) + j129.5$$

$$\underline{I}_{a2} = \frac{\underline{E}_{s2}}{jX_s} = \frac{-75.1 + j129.5}{j \cdot 0.5} = 258.9 + j150.2$$

$$= \underline{\underline{299.3 \text{ A} / 30.1^\circ}}$$

∴ Kapazitiv last, strømmen ligger foran spenningen.

Oppg. 6

(11)

a) $V_{GS} = 20 \cdot \frac{R_2}{R_1 + R_2} = 5$

$$20 \cdot R_2 = 5 \cdot 300 \cdot 10^3 + 5 \cdot R_2$$

$$R_2 = \frac{5 \cdot 300 \cdot 10^3}{20 - 5} \Omega = 100 \cdot 10^3 \Omega = \underline{\underline{100 \text{ k}\Omega}}$$


b) $20 = i_D \cdot R_D + V_{DS} = i_D \cdot 18 + V_{DS}$

$i_D = 0$ gir $V_{DS} = 20 \text{ V}$

$V_{DS} = 0$ " $i_D = \frac{20}{18} \text{ A} = 1.111 \text{ A}$

Arbeidslinje, se figur

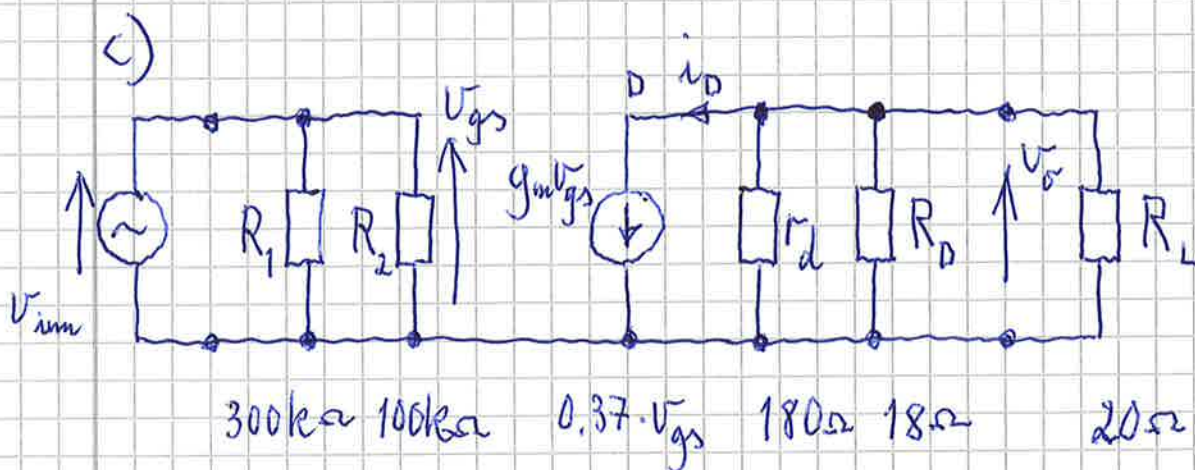$V_{DSQ} \approx 10 \text{ V}$, $I_{DQ} \approx 0.6 \text{ A}$




d) $R_L' = \left[\frac{1}{180} + \frac{1}{18} + \frac{1}{20} \right]^{-1} \Omega = 9.0 \Omega$

$V_a \approx -g_m V_{gs} \cdot R_L' = -0.37 \cdot 9 \cdot V_{inn}$, $V_{gs} = V_{inn}$

$\approx -0.37 \cdot 9 \cdot 0.5 \sin(\omega t) = \underline{\underline{-1.665 \cdot \sin(\omega t) \text{ V}}}$

Oppg. 7

(12)

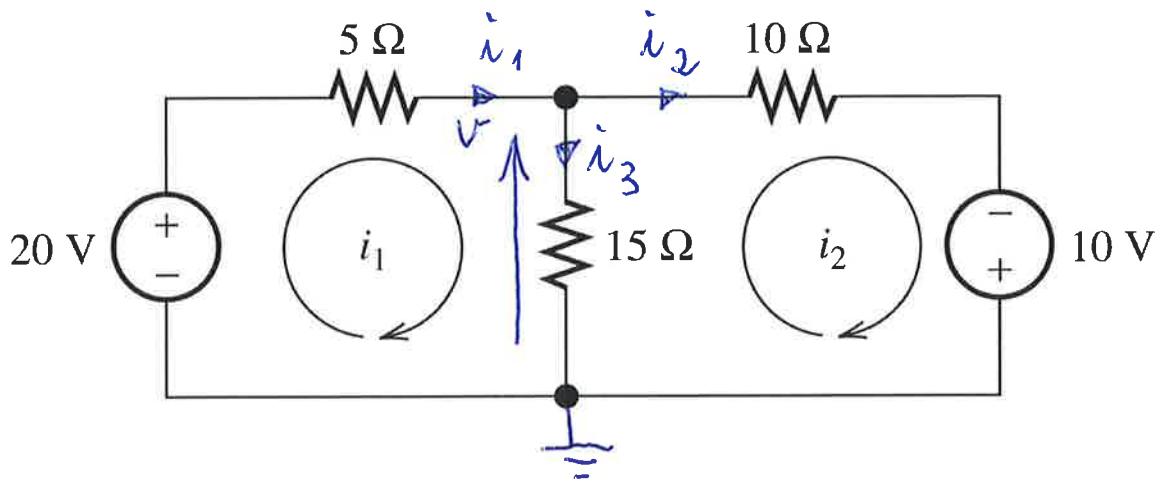

$$i_1 = \frac{20-v}{5}, \quad i_2 = \frac{v+10}{10}, \quad i_3 = \frac{v}{15}$$

Knutepunktanalyse:

$$i_1 - i_2 - i_3 = 0 \quad (\text{Kirchhoffs strømlov})$$

$$\frac{20-v}{5} - \frac{v+10}{10} - \frac{v}{15} = 0 \quad \parallel \cdot 30$$

$$-(6+3+2) \cdot v + 6 \cdot 20 - 3 \cdot 10 = 0$$

$$\Rightarrow \underline{\underline{v = \frac{90}{11} \text{ V}}}$$

$$\underline{\underline{i_1}} = \frac{20 - \frac{90}{11}}{5} = \underline{\underline{\frac{26}{11} \text{ A}}}, \quad \underline{\underline{i_2}} = \frac{\frac{90}{11} + 10}{10} = \underline{\underline{\frac{20}{11} \text{ A}}}, \quad \underline{\underline{i_3}} = \frac{\frac{90}{11 \cdot 15}}{1} = \underline{\underline{\frac{6}{11} \text{ A}}}$$

Op. no. 8 a) $n_m = 0 \Rightarrow E_A = 0$

$$E_A = V_T - R_A \cdot I_A = 0 \rightarrow R_A = \frac{V_T}{I_A} = \frac{12}{24} \Omega = \underline{\underline{0.5 \Omega}}$$

b) $P_{\text{utvr.}} = E_A \cdot I_A = (V_T - R_A \cdot I_A) \cdot I_A = V_T \cdot I_A - R_A \cdot I_A^2$

$$\frac{dP_{\text{utvr.}}}{dI_A} = V_T - 2R_A \cdot I_A = 0 \rightarrow I_A^{\text{max}} = \frac{V_T}{2R_A} = \frac{12}{2 \cdot 0.5} \text{ A} = 12 \text{ A}$$

$E_A = 6.0 \text{ V}$

$$\underline{\underline{P_{\text{utvr.}}^{\text{max}}}} = (12 - 0.5 \cdot 12) 12 \text{ W} = \underline{\underline{72 \text{ W}}}$$

c) $E_A = V_T - I_A \cdot R_A = (12 - 6 \cdot 0.5) \text{ V} = 9 \text{ V}$

$$E_A = K\Phi \cdot \omega_m = K\Phi n_m \cdot \frac{2\pi}{60} \Rightarrow$$

$$n_m = \frac{E_A \cdot 60}{K\Phi \cdot 2\pi} = \frac{9 \cdot 60}{(3/10) \cdot 2\pi} \text{ }^\circ/\text{min} = \underline{\underline{900^\circ/\text{min}}}$$